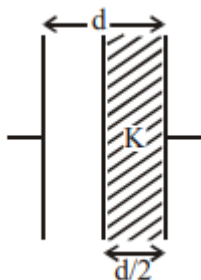


1.

A parallel plate capacitor having cross-sectional area A and separation d has air in between the plates. Now an insulating slab of the same area but thickness $d/2$ is inserted between the plates as shown in the figure having dielectric constant $K(=4)$. The ratio of new capacitance to its original capacitance will be?



1. 2: 1

2. 8: 5

3. 6: 5

4. 4: 1

2.

The capacitance of a parallel plate capacitor with air as medium is $6\mu\text{F}$. With the introduction of a dielectric medium, the capacitance becomes $30\mu\text{F}$. The permittivity of the medium is:

1. $1.77 \times 10^{-12} \text{ C}^2 \text{ N}^{-1} \text{ m}^{-2}$

2. $0.44 \times 10^{-10} \text{ C}^2 \text{ N}^{-1} \text{ m}^{-2}$

3. $5.00 \text{ C}^2 \text{ N}^{-1} \text{ m}^{-2}$

4. $0.44 \times 10^{-13} \text{ C}^2 \text{ N}^{-1} \text{ m}^{-2}$

3.

A parallel plate air capacitor is charged to a potential difference of V volts. After disconnecting the charging battery, the distance between the plates of the capacitor is increased using an insulating handle. As a result the potential difference between the plates:

1. decreases

2. does not change

3. becomes zero

4. increases

4.

A parallel plate air capacitor has capacity C , distance of separation between plates is d and potential difference V is applied between the plates. Force of attraction between the plates of the parallel plate air capacitor is?

1. $\frac{C^2 V^2}{2d}$

2. $\frac{CV^2}{2d}$

3. $\frac{CV^2}{d}$

4. $\frac{C^2 V^2}{2d^2}$

5.

The energy required to charge a parallel plate condenser of plate separation d and plate area of cross-section A such that the uniform electric field between the plates is E , is?

1. $\frac{1}{2} \epsilon_0 E^2 / Ad$

2. $\epsilon_0 E^2 / Ad$

3. $\epsilon_0 E^2 Ad$

4. $\frac{1}{2} \epsilon_0 E^2 Ad$

6.

The capacity of a parallel plate condenser is C . It's capacity when the separation between the plates is halved will be?

(1) $4C$

(2) $2C$

(3) $\frac{C}{2}$

(4) $\frac{C}{4}$

7.

The plates of a parallel plate condenser are pulled apart with a velocity v . If at any instant their mutual distance of separation is d , then the magnitude of the time rate of change of capacity depends on d as follows

(1) $1/d$

(2) $1/d^2$

(3) d^2

(4) d


8.

The capacity of a parallel plate condenser is $15 \mu F$, when the distance between its plates is 6 cm . If the distance between the plates is reduced to 2 cm , then the capacity of this parallel plate condenser will be?

- (1) $15 \mu F$
- (2) $30 \mu F$
- (3) $45 \mu F$
- (4) $60 \mu F$

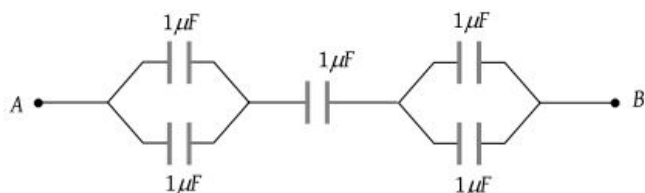9.


The equivalent capacitance between A and B is?



- (1) $2 \mu F$
- (2) $3 \mu F$
- (3) $5 \mu F$
- (4) $0.5 \mu F$

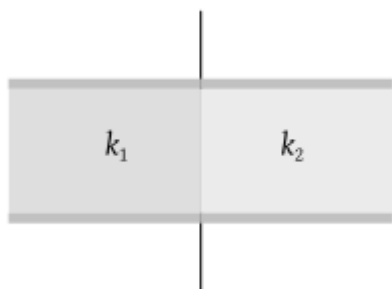10.

A parallel plate condenser is filled with two dielectrics as shown. Area of each plate is $A \text{ metre}^2$ and the separation is $t \text{ metre}$. The dielectric constants are k_1 and k_2 respectively. Its capacitance in farad will be?



- (1) $\frac{\epsilon_0 A}{t} (k_1 + k_2)$
- (2) $\frac{\epsilon_0 A}{t} \cdot \frac{k_1 + k_2}{2}$
- (3) $\frac{2\epsilon_0 A}{t} (k_1 + k_2)$
- (4) $\frac{\epsilon_0 A}{t} \cdot \frac{k_1 - k_2}{2}$

11.

Three capacitors of capacitances $3 \mu F$, $9 \mu F$ and $18 \mu F$ are connected once in series and another time in parallel. The ratio of equivalent capacitance in the two cases $\left(\frac{C_s}{C_p}\right)$ will be?

- (1) $1 : 15$
- (2) $15 : 1$
- (3) $1 : 1$
- (4) $1 : 3$


12.

A parallel plate capacitor of capacitance C is connected to a battery and is charged to a potential difference V . Another capacitor of capacitance $2C$ is connected to another battery and is charged to potential difference $2V$. The charging batteries are now disconnected and the capacitors are connected in parallel to each other in such a way that the positive terminal of one is connected to the negative terminal of the other. The final energy of the configuration is?

- (1) Zero
- (2) $\frac{25CV^2}{6}$
- (3) $\frac{3CV^2}{2}$
- (4) $\frac{9CV^2}{2}$

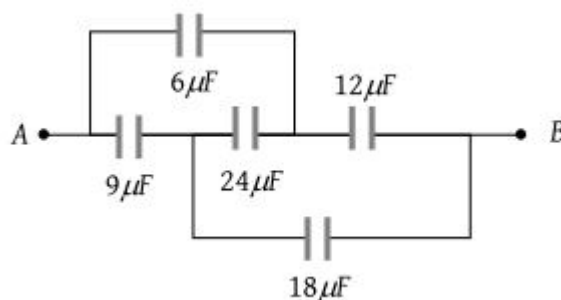13.

In the connections shown in the adjoining figure, the equivalent capacity between A and B will be?



- (1) $10.8 \mu F$
- (2) $69 \mu F$
- (3) $15 \mu F$
- (4) $10 \mu F$

14.

Two capacitances of capacity C_1 and C_2 are connected in series and potential difference V is applied across it. Then the potential difference across C_1 will be?

- (1) $V \frac{C_2}{C_1}$
- (2) $V \frac{C_1+C_2}{C_1}$
- (3) $V \frac{C_2}{C_1+C_2}$
- (4) $V \frac{C_1}{C_1+C_2}$


15.

A series combination of n_1 capacitors, each of value C_1 , is charged by a source of potential difference $4V$. When another parallel combination of n_2 capacitors, each of value C_2 , is charged by a source of potential difference V , it has the same (total) energy stored in it, as the first combination has. The value of C_2 , in terms of C_1 , is then

- (1) $\frac{2C_1}{n_1 n_2}$
- (2) $16 \frac{n_2}{n_1} C_1$
- (3) $2 \frac{n_2}{n_1} C_1$
- (4) $\frac{16C_1}{n_1 n_2}$

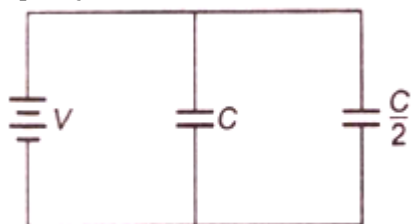16.

Two condensers, one of capacity C and the other of capacity $C/2$ are connected to a V volt battery, as shown.



The work done in charging fully both the condensers is?

1. $2 CV^2$
2. $\frac{1}{4} CV^2$
3. $\frac{3}{4} CV^2$
4. $\frac{1}{2} CV^2$

17.

100 capacitors each having a capacity of $10 \mu F$ are connected in parallel and are charged by a potential difference of $100 kV$. The energy stored in the capacitors and the cost of charging them, if electrical energy costs 108 paise per kWh , will be?

- (1) 10^7 joule and 300 paise
- (2) 5×10^6 joule and 300 paise
- (3) 5×10^6 joule and 150 paise
- (4) 10^7 joule and 150 paise


18.

The capacities of two conductors are C_1 and C_2 and their respective potentials are V_1 and V_2 . If they are connected by a thin wire, then the loss of energy will be given by

- (1) $\frac{C_1 C_2 (V_1 + V_2)}{2(C_1 + C_2)}$
- (2) $\frac{C_1 C_2 (V_1 - V_2)}{2(C_1 + C_2)}$
- (3) $\frac{C_1 C_2 (V_1 - V_2)^2}{2(C_1 + C_2)}$
- (4) $\frac{(C_1 + C_2)(V_1 - V_2)}{C_1 C_2}$

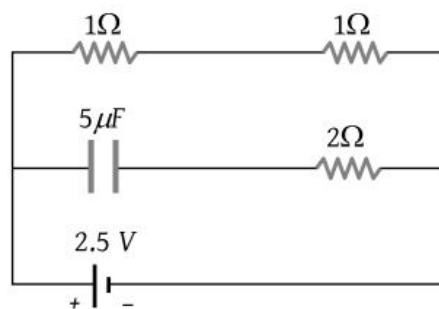19.


A capacitor of capacitance $5 \mu F$ is connected as shown in the figure. The internal resistance of the cell is 0.5Ω . The amount of charge on the capacitor plate is?



- (1) $0 \mu C$
- (2) $5 \mu C$
- (3) $10 \mu C$
- (4) $25 \mu C$

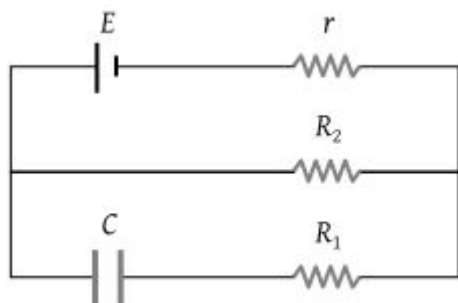20.

In the given figure each plate of capacitance C has partial value of charge?



- (1) CE
- (2) $\frac{CER_1}{R_2 - r}$
- (3) $\frac{CER_2}{R_2 + r}$
- (4) $\frac{CER_1}{R_1 - r}$

[Fill OMR Sheet](#)