


1.

The temperature coefficient of resistance of a wire is $2 \times 10^{-5} \text{ } ^\circ\text{C}^{-1}$. If its temperature is increased by 200°C , then the percentage increase in its resistance will be:

1. 2%
2. 0.2%
3. 4%
4. 0.4%

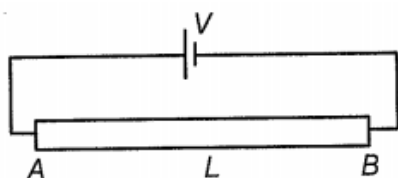2.


When the battery of emf V is applied across a conductor AB, the drift speed of electrons through the conductor is v . If the battery is replaced by a battery of emf $\frac{V}{2}$, then the new drift speed of free electrons will be:



1. v
2. $\frac{v}{2}$
3. $2v$
4. Zero

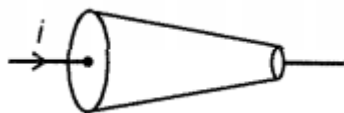3.

The current passes through a wire of variable cross-section in steady-state as shown. Then incorrect statement is:



- (1) Current density increases in the direction of the current.
- (2) Potential increases in the direction of the current.
- (3) Electric field increases in the direction of the current.
- (4) Drift speed increases in the direction of the current.

4.

The current in a wire varies with time according to the equation $I = 4 + 2t$, where I is in ampere and t is in sec. The quantity of charge which has passed through a cross-section of the wire during the time $t = 2$ sec to $t = 6$ sec will be:

- (1) 60 coulomb
- (2) 24 coulomb
- (3) 48 coulomb
- (4) 30 coulomb


5.

The length of a conductor is doubled keeping the volume constant. Percentage increase in its resistance is:


- (1) 100%
- (2) 200%
- (3) 300%
- (4) 400%

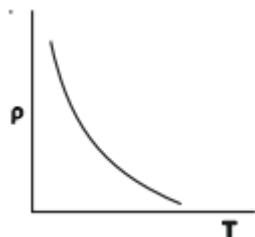6.


Which of the following graph represents the variation of resistivity (ρ) with temperature (T) for copper?




(1)

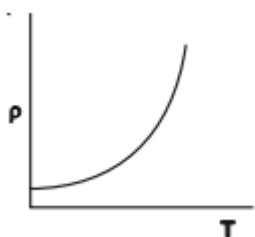

(2)

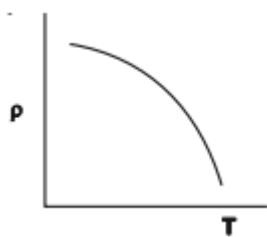


(3)

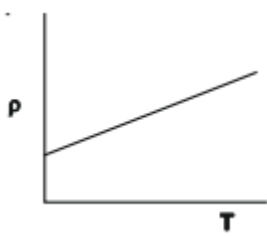

(4)

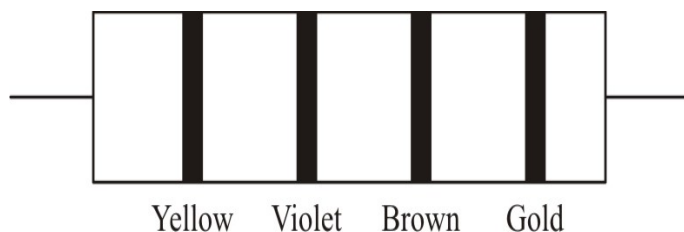7.

The colour code of resistance is given below:



The values of resistance and tolerance, respectively are:

1. 47 k Ω , 10%
2. 4.7 k Ω , 5%
3. 470 Ω , 5%
4. 470 k Ω , 5%

8.

A carbon resistor of (47 ± 4.7) k Ω is to be marked with rings of different colours for its identification. The colour code sequence will be:

1. Violet - Yellow - Orange - Silver
2. Yellow - Violet - Orange - Silver
3. Yellow - Green - Violet - Gold
4. Green - Orange - Violet - Gold

9.

The smallest resistance that can be obtained by the combination of n resistors each of resistance R is:

1. n^2R
2. nR
3. $\frac{R}{n^2}$
4. $\frac{R}{n}$


10.

The resultant resistance value of n resistors, each of r ohms and connected in series is x. When those n resistors are connected in parallel, the resultant value is

1. $\frac{x}{n}$
2. $\frac{x}{n^2}$
3. n^2x
4. nx

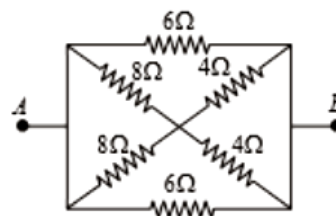11.


In the circuit shown in the figure, the effective resistance between A and B is:



1. 2 Ω
2. 4 Ω
3. 6 Ω
4. 8 Ω

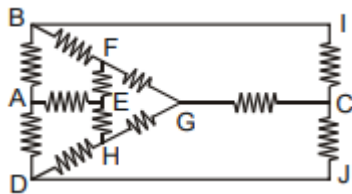12.


Find the equivalent resistance between A and E (the value of each resistor is R).



- (1) $\frac{7}{12}R$
- (2) $\frac{7}{13}R$
- (3) $\frac{7}{15}R$
- (4) $\frac{8}{13}R$

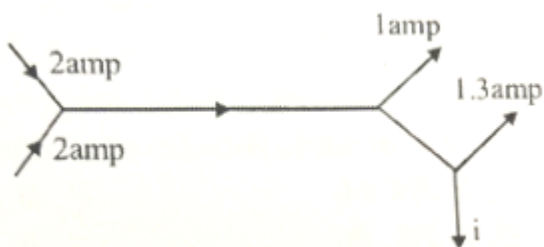13.


The figure below shows currents in a part of the electric circuit. The current 'i' is:



1. 1.7 amp
2. 3.7 amp
3. 1.3 amp
4. 1 amp

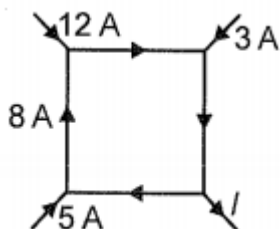14.


The current I in the circuit shown below is:



1. -3 A
2. 3 A
3. 13 A
4. 20 A

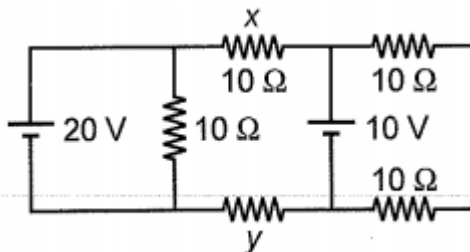15.


What is the ratio of currents flowing in the resistors x and y of resistance 10Ω each?



1. 1
2. 0.5
3. 1.5
4. 2.0

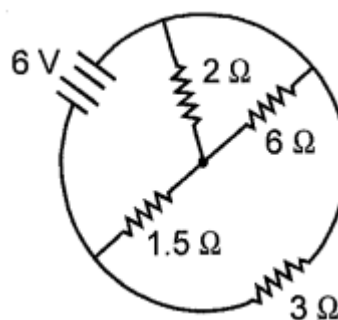16.


The total current supplied to the circuit by the battery in the given circuit is:



1. 1 A
2. 2 A
3. 4 A
4. 6 A

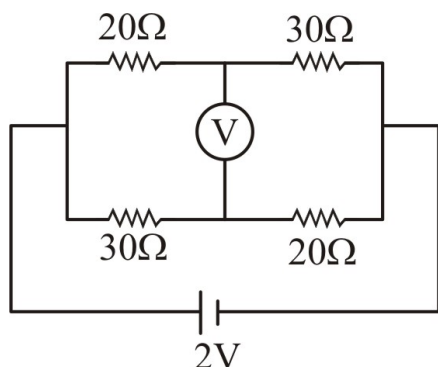17.


The reading of an ideal voltmeter in the circuit shown is:



1. 0.6 V
2. 0 V
3. 0.5 V
4. 0.4 V

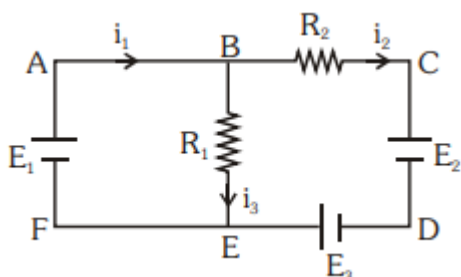18.


For the circuit given below, the Kirchoff's loop rule for the loop BCDEB is given by the equation:



1. $-i_2 R_2 + E_2 - E_3 + i_3 R_1 = 0$
2. $i_2 R_2 + E_2 - E_3 - i_3 R_1 = 0$
3. $i_2 R_2 + E_2 + E_3 + i_3 R_1 = 0$
4. $-i_2 R_2 + E_2 + E_3 + i_3 R_1 = 0$

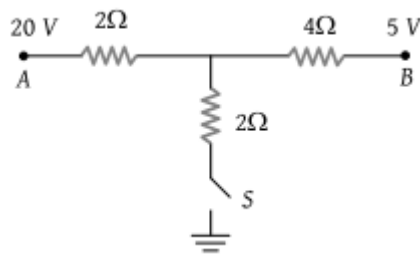19.


As the switch S is closed in the circuit shown in the figure, the current passed through it is:



- (1) 4.5 A
- (2) 6.0 A
- (3) 3.0 A
- (4) Zero

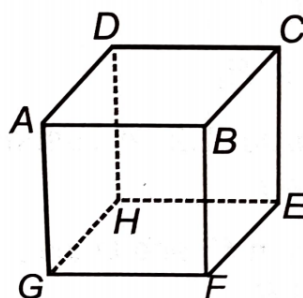20.

Twelve wires of equal resistance R are connected to form a cube. The effective resistance between two diagonal ends A and E will be:



1. $\frac{5R}{6}$
2. $\frac{6R}{5}$
3. 12R
4. 3R

[Fill OMR Sheet*](#)

*If above link doesn't work, please go to test link from where you got the pdf and fill OMR from there