

1.

Three resistances P, Q, R, each of $2\ \Omega$ and an unknown resistance S form the four arms of a Wheatstone bridge circuit. When the resistance of $6\ \Omega$ is connected in parallel to S, the bridge gets balanced. What is the value of S?

1. $2\ \Omega$
2. $3\ \Omega$
3. $6\ \Omega$
4. $1\ \Omega$


2.

A battery of internal resistance r , when connected across $2\ \Omega$ resistor supplies a current of 4 A . When the same battery is connected across a $5\ \Omega$ resistor, it supplies a current of 2 A . The value of internal resistance r is:

1. $2\ \Omega$
2. $1\ \Omega$
3. $0.5\ \Omega$
4. zero Ω

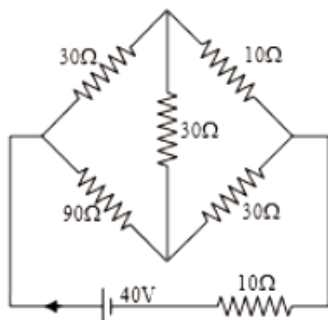3.


In the circuit shown in the figure, the current supplied by the battery is:



1. 2 A
2. 1 A
3. 0.5 A
4. 0.4 A

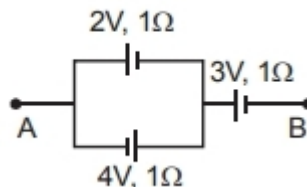4.


The potential difference between points A and B is:



1. 2 V
2. 6 V
3. 4 V
4. 3 V

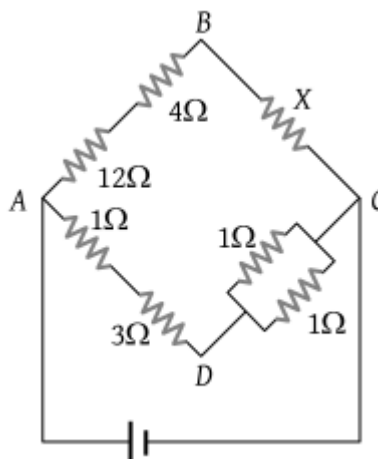5.

In the circuit shown in the adjoining figure, the potential difference between B and D is zero, the unknown resistance is:



- (1) $4\ \Omega$
- (2) $2\ \Omega$
- (3) $3\ \Omega$
- (4) EMF of a cell is required to find the value of X

6.

A coil heating a bucket full of water raises the temperature by 5°C in 2 min. If the current in the coil is doubled, what will be the change in temperature of water in 1 min?

Consider no losses of heat to surroundings.

1. 10°C
2. 5°C
3. 20°C
4. 15°C


7.

A 220 V, 1000 W bulb is connected across a 110 V mains supply. The power consumed is:

1. 1000 W
2. 750 W
3. 500 W
4. 250 W

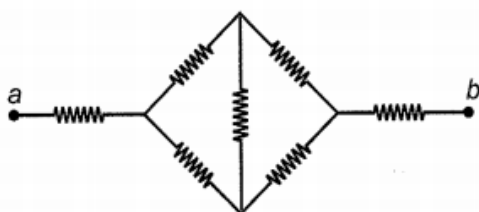8.


What is the equivalent resistance between points a and b, if the value of each resistance is R?



1. 7 R
2. 5 R
3. 4 R
4. 3 R

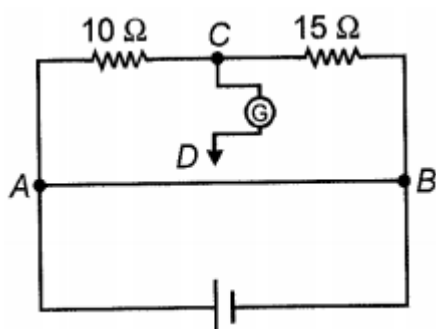9.

The wire AB shown in the figure has a uniform cross-section area and is 100 cm long. Where should the terminal D of the galvanometer be connected to the wire to get zero deflection in the galvanometer?



1. 40 cm from A
2. 50 cm from A
3. 40 cm from B
4. 80 cm from B

10.

Two cells of e.m.f. E and internal resistance r_1 and r_2 are connected in series through an external resistance R. The value of R for which the potential difference across one of the cells becomes zero will be:

1. $\frac{r_1 r_2}{r_1 + r_2}$
2. $r_1 + r_2$
3. $|r_2 - r_1|$
4. $\frac{r_1}{r_2}$


11.

Two heater wires of equal length are first connected in series and then in parallel. The ratio of heat production in the two cases is:

1. 1 : 3
2. 1 : 2
3. 1 : 8
4. 1 : 4

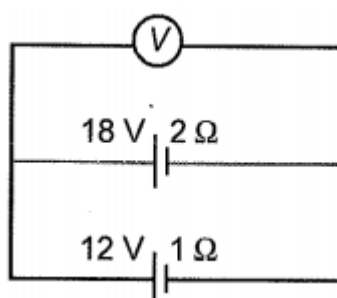12.

Two batteries, one of emf 18 V and internal resistance 2Ω and the other of emf 12 V and internal resistance 1Ω are connected as shown. Reading of the voltmeter is: (if voltmeter is ideal)



1. 14 V
2. 15 V
3. 18 V
4. 30 V


13.

A current of 2 A is to be sent through a resistor of $5\ \Omega$. Number of cells required in series, if each has emf 2 V and internal resistance $0.5\ \Omega$, is

1. 40
2. 30
3. 20
4. 10

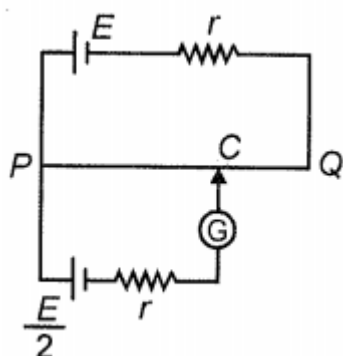14.

The potentiometer wire PQ is 100 cm long and its resistance is $2r$, where r is the internal resistance of the battery. The balancing length PC is equal to:



1. 25 cm
2. 75 cm
3. 50 cm
4. 40 cm

15.

In a potentiometer arrangement, a cell of emf 1.25 V gives a balance point at 35.0 cm length of the wire. If the cell is replaced by another cell and the balance point shifts to 63.0 cm, then the emf of the second cell is:

- (1) 1.27 V
- (2) 2.25 V
- (3) 3.27 V
- (4) 3.25 V

16.

The storage battery of a car has an emf of 12 V. If the internal resistance of the battery is $0.4\ \Omega$, what is the maximum current that can be drawn from the battery?

- (1) 30 A
- (2) 20 A
- (3) 10 A
- (4) 40 A

17.


A battery of emf 10 V and internal resistance $3\ \Omega$ is connected to a resistor. If the current in the circuit is 0.5 A, what is the terminal voltage of the battery when the circuit is closed?

- (1) 10 V
- (2) 8.5 V
- (3) 1.5 V
- (4) 7.2 V

18.

According to this diagram, the potential difference across the terminals is:

(internal resistance of cell = r)

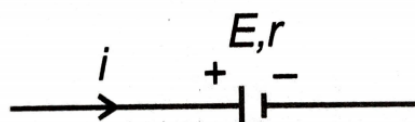

1. $V = E - ir$
2. $V = E + ir$
3. $V = E$
4. Zero


19.

Two cells of e.m.f. E_1 and E_2 are joined in series and the balancing length of the potentiometer wire is 625 cm. If the terminals of E_1 are reversed, the balancing length obtained is 125 cm. Given $E_2 > E_1$, the ratio $E_1:E_2$ will be:

1. 2 : 3
2. 5 : 1
3. 3 : 2
4. 1 : 5

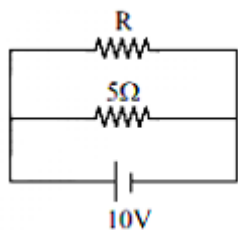20.

The power dissipated in the circuit shown in the figure is 30 Watts. The value of R is:



1. $15\ \Omega$
2. $10\ \Omega$
3. $30\ \Omega$
4. $20\ \Omega$

[Fill OMR Sheet*](#)

*If above link doesn't work, please go to test link from where you got the pdf and fill OMR from there